

**Indian Maritime University**  
( A Central University, Govt of India)  
B Sc (Nautical Science)  
June 2018 End Semester Examinations  
Semester-II  
UG21T3202 - Applied Physics & Electricity

Duration:3 Hrs

Max Marks:70 Marks

Date: 07.06.2018

Pass Marks:35 Marks

**PART-A**

**QUESTION NO.1 IS COMPULSORY**

(5×2=10 Marks)

- 1.a) Define coefficient of coupling.
- b) Define resonant frequency.
- c) State Kirchoff voltage law.
- d) State Thevenin's theorem.
- e) Define Active power.

**PART-B**

**ATTEMPT ANY SIX QUESTIONS OUT OF EIGHT.**

(6×10=60 Marks)

- 2.a) State the faraday's laws of electromagnetic induction. (5 Marks)
- b) A solenoid of length 1 m and 0.05 m diameter has 500 turns. If a current of 2A passes through the coil, calculate (i) the coefficient of self induction of the coil and (ii) the magnetic flux linked with a the coil. (5 Marks)
3. a) Define power factor, quality factor and band width of an ac circuit. (5 Marks)
- b) An AC voltage represented by  $e = 310 \sin 314 t$  is connected in series to a 24  $\Omega$  resistor, 0.1 H inductor and a 25  $\mu\text{F}$  capacitor. Find the value of the peak voltage, rms voltage, frequency, reactance of the circuit, impedance of the

circuit and phase angle.  
(5 Marks)

(5 Marks)

4. a) Explain Schering bridge network and arrive at the expression of unknown resistance and unknown capacitance. (5 Marks)

b) The four arms of a Hay's a.c bridge are arranged as follows:

AB is a coil of unknown impedance.

BC is a non-reactive resistor of  $1000\Omega$ .

CD is a non-reactive resistor of  $833\Omega$  in series with a standard capacitor of  $0.38\mu\text{F}$ .


DA is a non-reactive resistor of  $16,800\Omega$ .

If the supply frequency is 50 Hz. Determine the inductance and the resistance at the balance condition. (5 Marks)

5.a) State and explain Norton's theorem. (5 Marks)

(5 Marks)

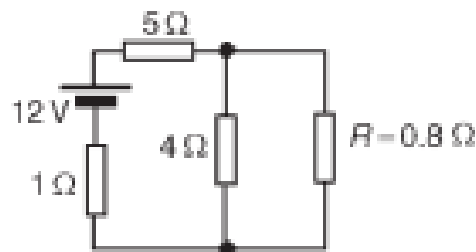b) For the network shown below, determine the current in the  $0.8\Omega$  resistor using Thevenin's theorem. (5 Marks)



(a)

6.a) Explain thermo electric effect. (5 Marks)

(5 Marks)

b) An ac generator consists of a coil of 10,000 turns and of area  $100\text{ cm}^2$ . The coil rotates at an angular speed of 140 rpm in a uniform magnetic field of  $3.6 \times 10^{-2}\text{ T}$ . Find the maximum value of the emf induced. (5 Marks)

7.a) Explain how thermistor works, in finding the temperature coefficient of resistance. (5 Marks)

(5 Marks)

b) Define Accuracy and calibration. (5 Marks)

(5 Marks)

8. a) Explain with principle, construction and working of DC generator. (5 Marks)

b) In a desauty bridge network, arm 1 contains a  $2\text{ K}\Omega$  non inductive resistor, arm 3 contains a loss free  $2.4\ \mu\text{F}$  capacitor and arm 4 contains a  $5\text{ K}\Omega$  non inductive resistor. When the bridge is balanced. Determine the value of the capacitor contained in arm 2. (5 Marks)

9. Write short notes on any two. (2×5=10 Marks)

a) Millman theorem. (5 Marks)

b) Transducers. (5 Marks)

c) Capacitors in series and Parallel. (5 Marks)

d) Series type DC motor. (5 Marks)