

**INDIAN MARITIME UNIVERSITY**  
**Time Bound Assignment**  
**B Tech (ME) Arrear Examinations**  
**September/October 2020**  
**UG11T3104**  
**BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

---

Date: 15/09/2020  
Duration: 3 Hrs

Max Marks: 70  
Pass Marks: 35

---


**Part – A (compulsory)**  
**Answer the following (10x2=20 Marks)**

1. State Ohm's Law.
2. The three terminals of delta connected network are 1, 2, and 3. The resistances between the two terminals are  $R_{12}$ ,  $R_{23}$ , and  $R_{31}$  respectively. Give the expressions to convert them into equivalent resistances  $R_1$ ,  $R_2$ , and  $R_3$  of star connected network.
3. State Coulomb's second law of electrostatics and write the mathematical expression.
4. Define Root Mean Square Value of an alternating current.
5. Give the relation between the line voltage and phase voltage as well as the line current and phase current of a star connected three-phase a.c. circuit.
6. The reluctance of a magnetic circuit is  $10^5$  AT/Wb and the excitation coil has 200 turns. Find the energy stored in the coil when the instantaneous current at  $t = 1$  second is one Ampere.
7. Name the methods to produce damping torque in measuring instruments.
8. Give the classification of extrinsic semiconductors. How are they formed?
9. What is PN junction? How is it formed?
10. What is Bipolar Junction Transistor? How are its terminals named?

**Part – B**

**Answer any 5 out of 7 questions (5 x 10= 50 marks)**

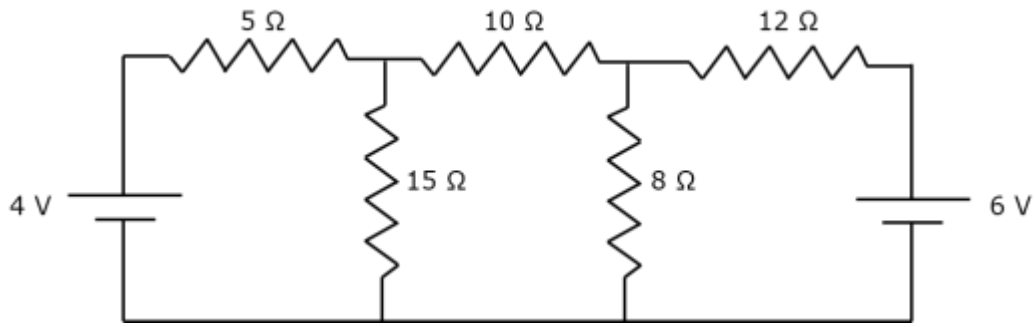11. a. A network is arranged as shown in the figure below. Determine the value of current in the  $8 \Omega$  resistor, using mesh equations. **(5 Marks)**



**b.** A resistance  $R$  is connected in series with a parallel circuit comprising two resistors 12 ohms and 8 ohms respectively. The total power dissipated in the circuit is 70 Watts when the applied voltage is 22 Volts. Calculate the value of  $R$ . **(5 Marks)**

**12.** What is lead acid battery? Describe the construction and its working principle. **(10 Marks)**

**13.** A series RLC circuit with  $R = 10$  ohms,  $L = 10\text{mH}$  and  $C = 1\mu\text{F}$  has an applied voltage of 200 V at resonant frequency. Calculate the resonant frequency, the current in the circuit, quality factor and bandwidth. **(10 Marks)**

**14.** Discuss the working principle of attraction type moving iron instruments. Also, derive an expression for the deflecting torque. **(10 Marks)**

**15.** Explain how two-wattmeter method is used to measure three phase power in star and delta connected balanced loads. **(10 Marks)**

**16. a.** Draw and explain the characteristics of Zener diode. **(6 marks)**

**b.** The arms of an a.c. Maxwell bridge are arranged as follows: AB is a non- inductive resistance of  $1,000 \Omega$  in parallel with a capacitor of capacitance  $0.5 \mu\text{F}$  , BC is a non-inductive resistance of  $600 \Omega$  CD is an inductive impedance (unknown) and DA is a non- inductive resistance of  $400 \Omega$  . If balance is obtained under these conditions, find the value

of the resistance and the inductance of the branch CD. A.C. voltage is applied across the branch AC. **(4 marks)**

**17. a.** Draw and explain the working of full wave bridge rectifier using PN junction diodes. **(5 Marks)**

**b.** Draw and explain the output characteristics of NPN transistor in CE configuration. **(5 Marks)**

\* \* \* \* \*