

INDIAN MARITIME UNIVERSITY
(A Central University, Government of India)
END SEMESTER EXAMINATION DEC./JAN-2019-20
B.SC. (Nautical Science)
Semester: II
Nautical Electronics (UG21T3203)

Date: 06-01-2020

Maximum marks: 70

Time: 3 Hours

Pass marks: 35

PART-A: Compulsory question

- 1.a) Define PN junction diode. (2)
- b) Define current gain α and β of transistor. (2)
- c) State Barkhausen's criteria for oscillations. (2)
- d) What is the need for modulation. (2)
- e) What are the elements of RADAR system. (2)

PART-B

(Attempt any six questions out of eight)

- 2.a) What is rectifier? With a neat sketch, explain the working of a half wave rectifier. (5)
- b) Determine the output voltage for inverting and non-inverting amplifier circuit having $R_{in}=2.4\text{ K}\Omega$, $R_f =240\text{K}\Omega$ and input voltage $120\mu\text{V}$. Show the circuits as well. (5)
- 3.a) What is a transistor? Explain input and output characteristics of a NPN transistor in a common base configuration. (5)
- b) Classify the amplifiers according to the mode of operations. (5)
4. a) What is an oscillator? Compare it with an amplifier. (5)
- b) A tuned collector oscillator has a fixed inductance of $100\mu\text{H}$ and has to be tunable over the frequency band of 500 kHz to 1500 kHz. Find the range of variable capacitor to be used. (5)
- 5.a) Prove the Boolean Identities. (5)
 - a) $(A*B)*(A+B) = 0$
 - b) $(A*B) + (A+B) = 1$
- b) What are flip flop circuits? Explain basic flip flop circuit using transistor. (5)

6. a) What is frequency modulation? How it is different from amplitude modulation? (5)
- b) A sinusoidal carrier voltage frequency 1000 kHz is amplitude modulated by a sinusoidal voltage frequency 20 kHz, resulting in maximum and minimum modulated carrier amplitudes of 100 V and 50 V respectively. Calculate,
- i. Frequency of lower and upper side bands.
 - ii. Modulation index.
 - iii. Amplitude of each side band. (5)
7. a) Define Modulation Index and detection efficiency. (5)
- b) Show the circuit of Hartley oscillator and determine the operating frequency and feed back fraction if $L_1=1000\mu\text{H}$, $L_2=100\mu\text{H}$ and $C=20\text{PF}$. (5)
8. a) Draw and explain diagram of Radio Broadcast Transmitter for AM Radio Broadcasting? (5)
- b) Draw and explain block diagram of FM Radio Receiver? (5)
9. a) Draw block schematic and explain basic concepts of RADAR. (5)
- b) Write short note on Radio Direction Finder. (5)
