

Indian Maritime University
(A Central University, Govt of India)

Sep/Oct'25 SE

Programme Name: B Tech (ME)

Semester: I

Subject Code: UG11T5105

Subject Name: BASIC ELECTRICAL TECHNOLOGY

Date: 13.09.2025	Max Marks: 70
Duration: 03 Hrs	Pass Marks: 35

General Instructions

- (i) All Sections (A, B & C) are to be attempted.
- (ii) Options, if any, are specified in respective section.
- (iii) Only non-programmable scientific calculators can be used for solving the problems

Section A

Ten MCQs/Fill in the Blanks of 01 Mark each – Choose the correct answer as applicable.

1. The Internal resistance of ideal current source is

a) 0	b) ∞	c) Very low but finite	d) None of the above
------	-------------	------------------------	----------------------

2. According to KVL, the algebraic sum of all IR drops and EMFs in any closed loop of a network is always

a) zero	b) positive	c) negative	d) determined by battery e.m.fs
---------	-------------	-------------	---------------------------------

3. KVL deals with the conservation of?

a) mass	b) Momentum	c) Energy	d) Charge
---------	-------------	-----------	-----------

4. Relative permeability of vacuum is

a) $4\pi \times 10^{-7}$ H/m	b) 1 H/m	c) 1	d) $1/4\pi$
------------------------------	----------	------	-------------


5. The magnetic flux through a coil having a single turn is varying according to the relation: $\phi = (25t^3 + 10t^2 + 5t - 5)$ Wb. Determine the

- impedance of the coil (in ohm) If the induced current through the coil is 10 A at $t = 1$ sec?
- a)50 b)10 c)100 d)None of the above
6. The symbol j represents counterclockwise rotation of a vector through—degrees
- a)180 b)90 c)360 d)270
7. In a delta-connected system, the currents $I_R = I_B = I_Y = ?$
- a) I_{Ph} b) $2I_{Ph}$ c) $3I_{Ph}$ d) $4I_{Ph}$
8. The minimum number of wattmeters required for measurement of 3 phase power is
- a)1 b)2 c)3 d)4
9. The kWh meter can be classified as a/an _____ instrument
- a) deflecting b) digital c) recording d) indicating
- 10 Creeping in energy meter can avoided by _____
- a) reversing the polarity of the voltage b) drilling two diametrically opposite holes c) holding the disc d) increasing the friction

Section B

Five Questions of 02 Marks each.

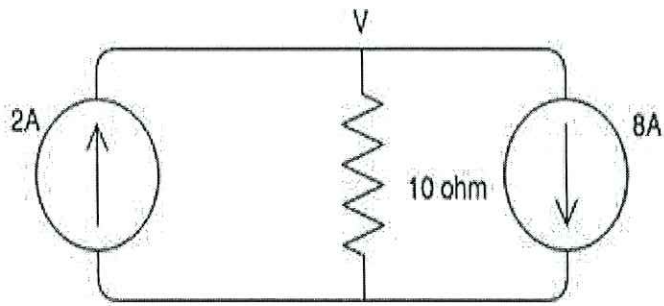
11. A current $i = 5 + 14.14 \sin (314 t + 45^\circ)$ is passed through a center-zero PMMC and moving iron instrument. What will be the reading of both the instruments?
12. A conductor of length 1 metre moves at right angles to a uniform magnetic field of flux density 1.5 Wb/m^2 with a velocity of 50 metre/second. Calculate the e.m.f. induced in it, when the conductor moves at an angle of 30° to the direction of the field.
13. How the RLC series circuit behaves for the frequencies above and below the resonant frequencies.
14. When is the force on a current-carrying conductor in a magnetic field zero?
15. Find the value of the node voltage V for the circuit given below.



Section C

Seven Questions of 10 Marks each of which any 05 questions to be answered.

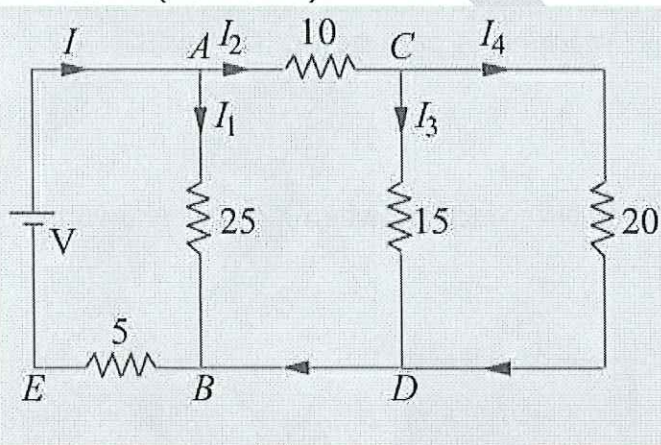16. In the circuit of Figure below, find the value of supply voltage V so that $20\text{-}\Omega$ resistor can dissipate 180 W (10 marks)




17. (a) Write short note on the following

- (i) Faraday's law of Electromagnetic Induction
- ii) Lenz's Law

(2+2=4 marks)

(b) Derive the expression for Force on current-carrying conductor lying in the magnetic field. (6 marks)

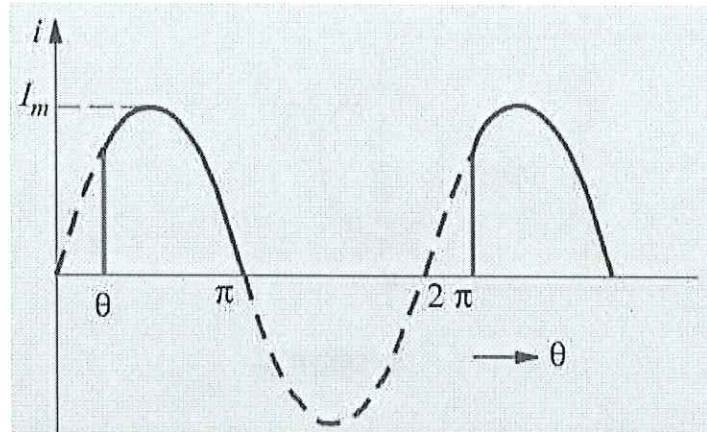
18.a) The waveform of an output current is as shown in Fig. below It consists of a portion of the positive half cycle of a sine wave between the angle θ and 180° . Determine the effective value for $\theta = 30^\circ$. (5 marks)



b) A three phase 400-V, 50 Hz, a.c. supply is feeding a three phase delta connected load with each phase having a resistance of 25 ohms, an inductance of 0.15 H, and a capacitor of 120 microfarads in series. Determine the line current, volt-amp, active power and reactive volt-amp and draw the load network with proper marking of parameters (5 marks)


19. Find the Potential Difference between X and Y shown in the network.

(10 Marks)

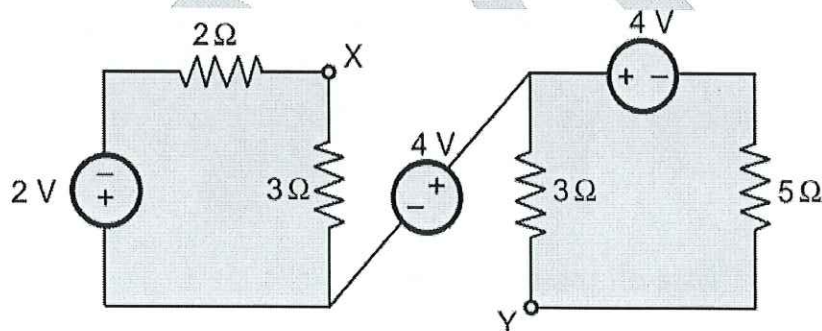

20. Calculate the power dissipated in a resistance of 10Ω . The waveform profile of current flowing through the resistance is shown in the figure having a peak value $A=10$.

(10 marks)

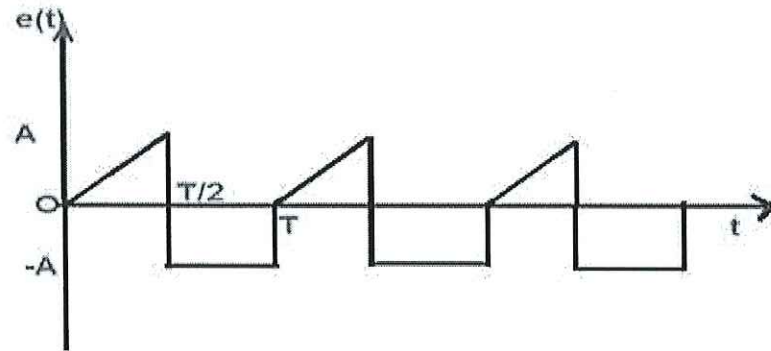

21. With a neat diagram, explain the construction and working of Dynamometer type Wattmeter. (10 marks)

22. (a) Three loads, each of resistance 30, are connected in star to a 415 V, 3-phase supply. Determine

- (i) the system phase voltage,
- (ii) the phase current
- (iii) the line current

(2+1+1=4 marks)

(b) Derive the formula for power factor calculation in case of two wattmeter method. What are the major limitations of two Wattmeter method.

(5+1=6 Marks)

